

www.mbsm.pro ,PICTURE, How to Make, Blinking Indicator, With relay 6v , Condensor 1000uf , battery 9v , and a simple led

written by mahdi miled | 3 January 2019

How to Make, Blinking Indicator, With relay 6v , Condensor 1000uf , battery 9v , and a simple led